 



LD – Second Internal Answer key

PART-B


2 (a) Design a 4 x 16 decoder using two 3 x 8 decoders.



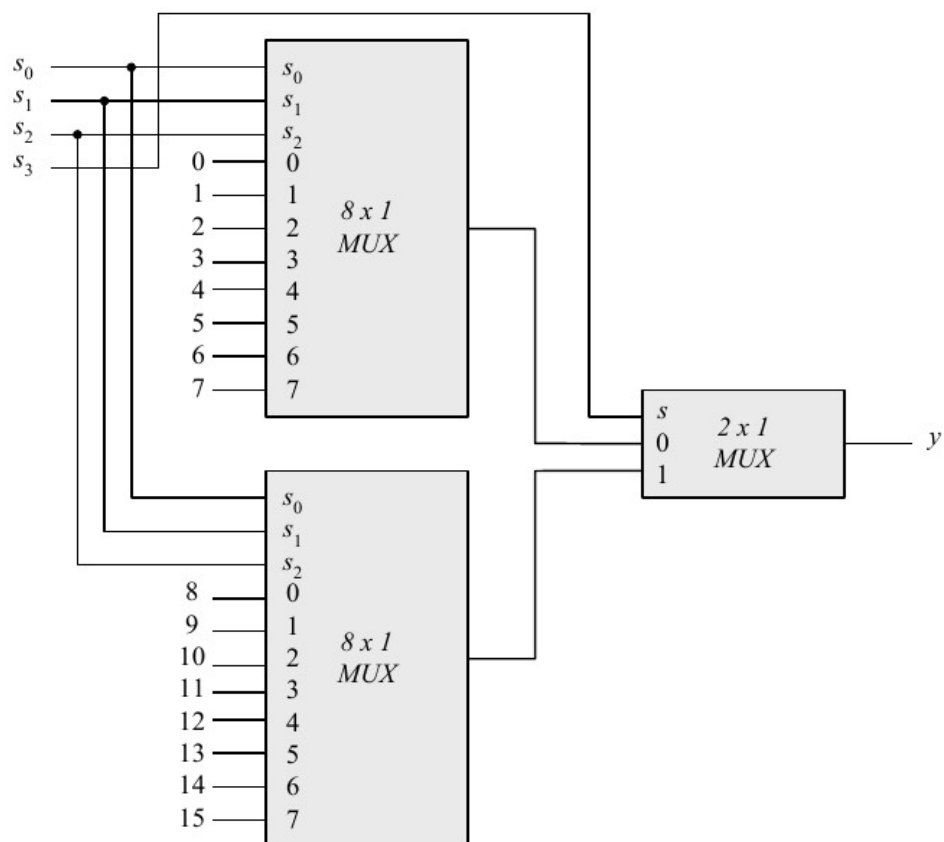(b) Construct a 16 x 1 multiplexer with two 8 x 1 and one 2 x 1 multiplexers.



 3. (a) Develop a synchronous 3-bit up/down counter with a Gray code sequence using J-K flip-flops. The counter should count up when an UP/DOWN control input is 1 and count down when the control input is 0.



Transition table for a J-K flip-flop.

Output Transitions		Flip-Flop Inputs	
Q_N	Q_{N+1}	J	K
0	→ 0	0	X
0	→ 1	1	X
1	→ 0	X	1
1	→ 1	X	0

Next-state table for 3-bit up/down Gray code counter.


Present State			Next State					
			$Y = 0$ (DOWN)			$Y = 1$ (UP)		
			Q_2	Q_1	Q_0	Q_2	Q_1	Q_0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	0	1	1
0	1	1	0	0	1	0	1	0
0	1	0	0	1	1	1	1	0
1	1	0	0	1	0	1	1	1
1	1	1	1	1	0	1	0	1
1	0	1	1	1	1	1	0	0
1	0	0	1	0	1	0	0	0

$Y = \text{UP}/\overline{\text{DOWN}}$ control input.


$$\begin{aligned}
 J_0 &= Q_2 Q_1 Y + Q_2 \bar{Q}_1 \bar{Y} + \bar{Q}_2 \bar{Q}_1 Y + \bar{Q}_2 Q_1 \bar{Y} & K_0 &= \bar{Q}_2 \bar{Q}_1 \bar{Y} + \bar{Q}_2 Q_1 Y + Q_2 \bar{Q}_1 Y + Q_2 Q_1 \bar{Y} \\
 J_1 &= \bar{Q}_2 Q_0 Y + Q_2 Q_0 \bar{Y} & K_1 &= \bar{Q}_2 Q_0 \bar{Y} + Q_2 Q_0 Y \\
 J_2 &= Q_1 \bar{Q}_0 Y + \bar{Q}_1 \bar{Q}_0 \bar{Y} & K_2 &= Q_1 \bar{Q}_0 \bar{Y} + \bar{Q}_1 \bar{Q}_0 Y
 \end{aligned}$$

3(b) Design a four-bit shift register with parallel load using D flip-flops. There are two control inputs: shift and load. When shift = 1, the content of the register is shifted by one position. New data are transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.


First stage of register:

 

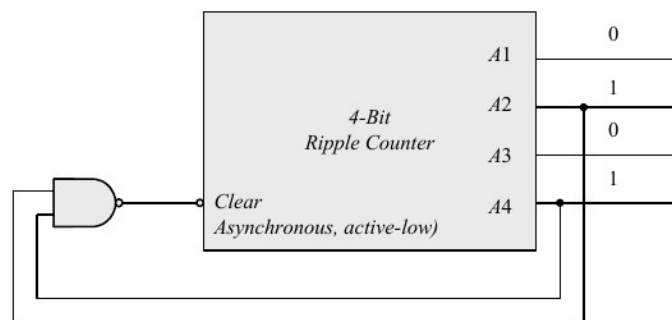
4{a} Show that a BCD ripple counter can be constructed using a four-bit binary ripple counter with asynchronous clear and a NAND gate that detects the occurrence of count 1010.



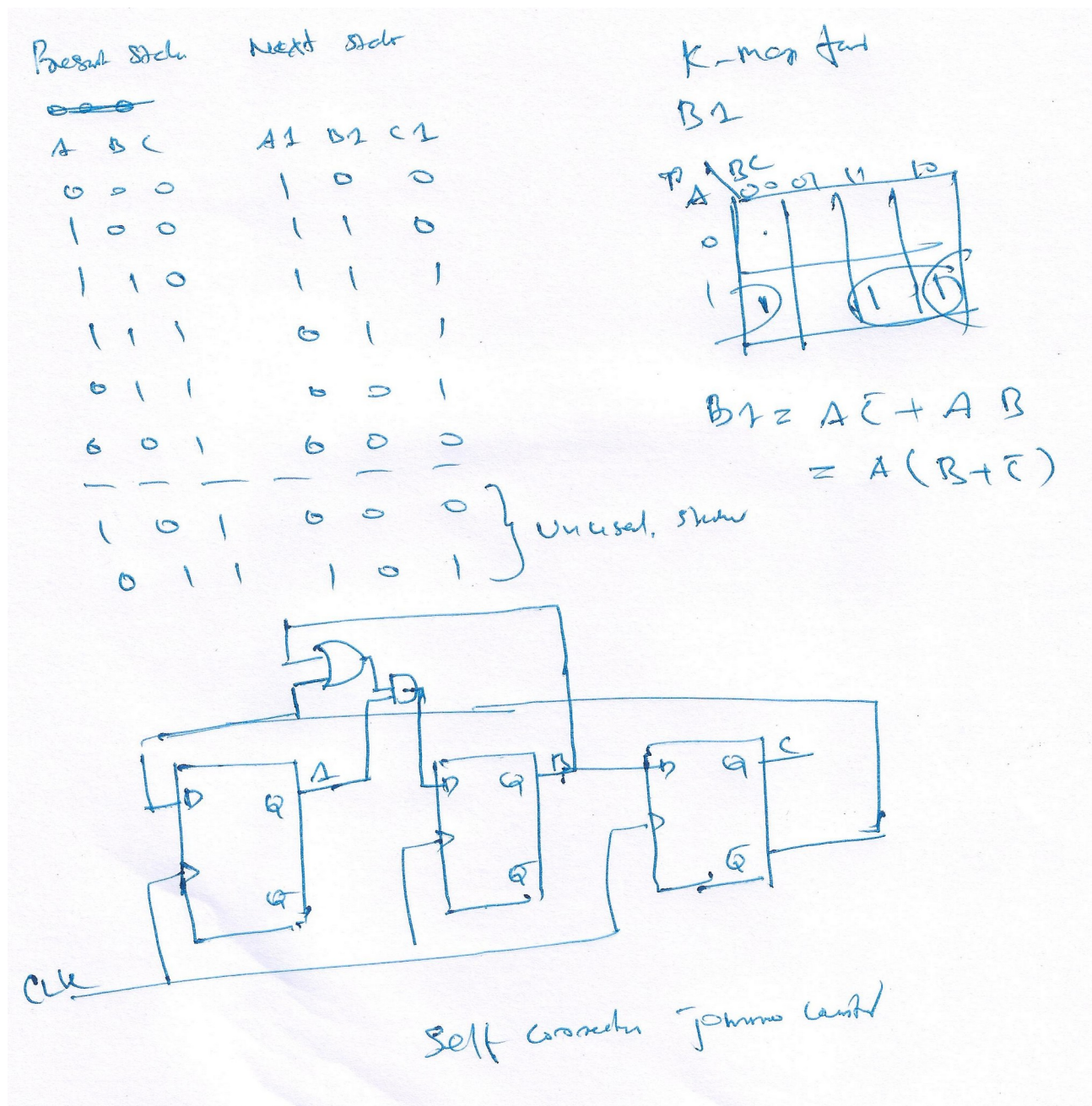4(b) Design a 3-bit self correcting Johnson counter



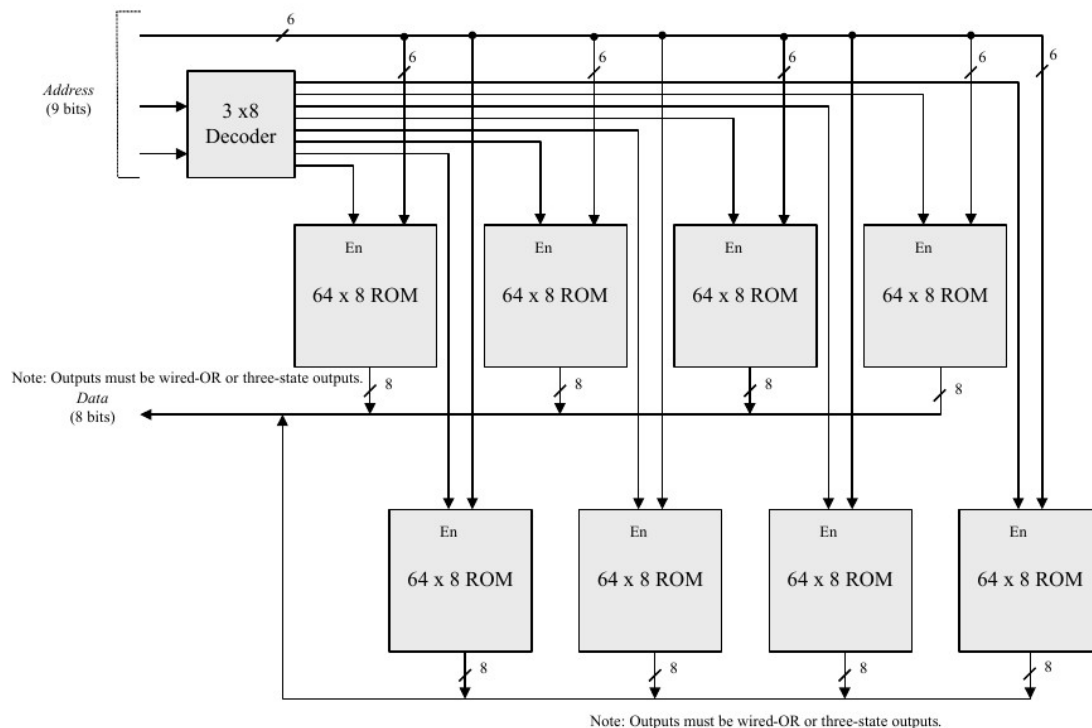5(a) Using 64×8 ROM chips with an enable input, construct a 512×8 ROM with eight chips and a decoder.



5(b) List the programming table for the BCD-to-excess-3-code converter for

(i) PAL

(ii) PL A

PLA

	Product term	Inputs $A B C D$	Outputs $F_1 F_2 F_3 F_4$
$w = A + BC + BD$	1	1 - - -	1 - - -
$w' = A'B' + A'C'D'$	2	- 1 1 -	1 1 - -
$x = B'C + B'D + BC'D'$	3	- 1 - 1	1 1 - -
$x' = B'C'D' + BC BD$	4	- 0 0 0	- 1 - -
$y = CD + C'D'$	5	- - 1 1	- - 1 -
$y' = C'D + CD'$	6	- - 0 0	- - 1 -
$z = D'$	7	- - - 0	- - - 1
$z' = D$			<u>$T C T T$</u>

Use w, x', y, z (7 terms)

AND			
Product	Inputs		
term	$A\ B\ C\ D$	Outputs	
1	1 - - -	$w = A + BC + BD$	PAL
2	- 1 1 -		
3	- 1 - 1		
4	- 0 1 -	$x = B'C + B'D + BC'D'$	
5	- 0 - 1		
6	- 1 0 0		
7	- - 1 1	$y = CD + C'D'$	
8	- - 0 0		
9	- - - -		
10	- - - 0	$z = D'$	
11	- - - -		
12	- - - -		